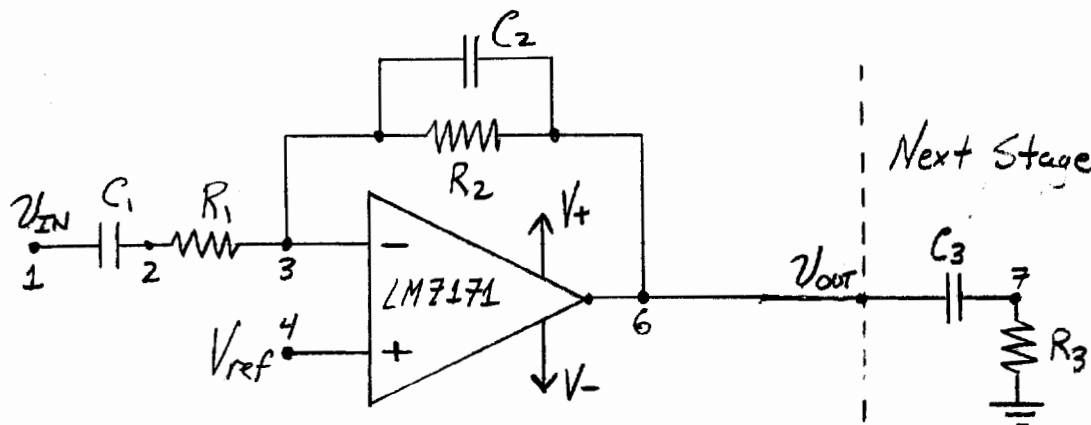


# Design of Op-Amp Stage for High Frequency and Stability

①



First we should lump the 6 passive components into 3 complex impedances,  $Z_1$ -3.

[1a]

$$Z_1 = R_1 - \frac{j}{\omega C_1} = R_1 \left(1 - j \frac{\omega_1}{\omega}\right),$$

[2a]

$$Z_2 = \frac{R_2}{j\omega C_2 (R_2 + j\omega C_2)} = R_2 \left(\frac{1}{1 + j \frac{\omega}{\omega_2}}\right),$$


[3a]

$$Z_3 = R_3 - \frac{j}{\omega C_3} = R_3 \left(1 - j \frac{\omega_3}{\omega}\right), \text{ where}$$

[1b, 2b, 3b]

$$\omega_1 = \frac{1}{R_1 C_1}, \quad \omega_2 = \frac{1}{R_2 C_2}, \quad \omega_3 = \frac{1}{R_3 C_3}$$

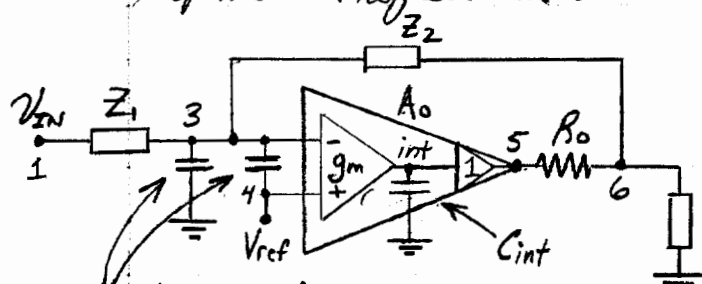Next we add parasitics to the ideal op-amp, which affect the high frequency response and reflect the LM7171.






$C_0$  Internally, the op-amp has a differential transconductance amplifier coupled to some parasitic capacitance  $C_{int}$  and an output voltage buffer; and that a high frequency pole is created.

$$A_o = \frac{V_5}{V_4 - V_3} = \frac{-j g_m}{Z_{in} C_{int} f} = \frac{-j}{|GB| f}$$

Typical input capacitance of IC and leads:


$$C_0 = 20pF$$

Texas Instruments  
LM7171

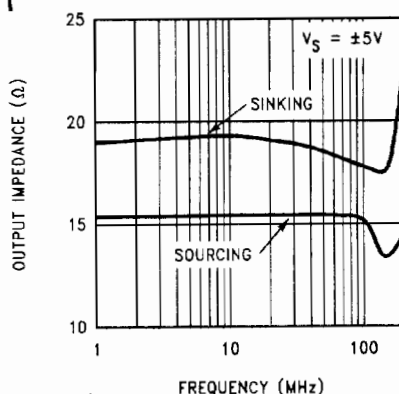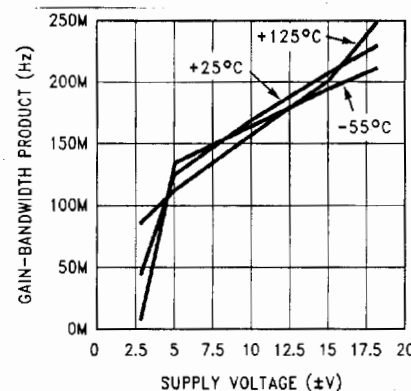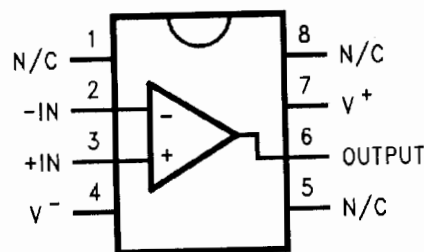

(2)

## AC Circuit Analysis

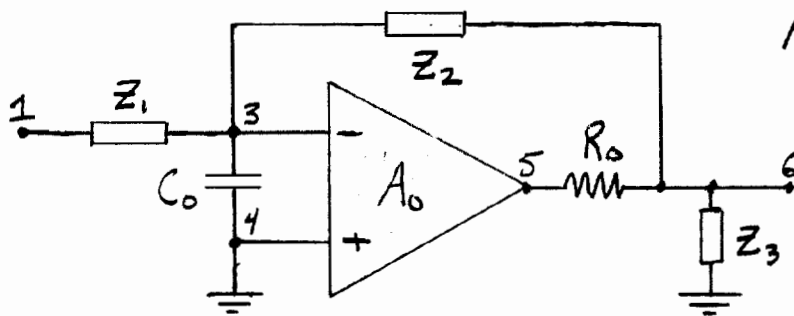

$$A_0 = \frac{-j}{|GB|f} = \frac{V_5}{V_4 - V_3}$$

$$V_5 = \frac{-j}{|GB|f} (V_4 - V_3)$$

KCL at node 3:

$$\frac{V_3 - V_1}{Z_1} + \frac{V_3}{\frac{1}{j\omega C_0}} + \frac{V_3 - V_5}{Z_2} = 0$$

[4.1]

$$V_3 \left[ \frac{1}{Z_1} + \frac{1}{Z_2} + j\omega C_0 \right] + V_5 \left[ \frac{-1}{Z_2} \right] = V_1 \left[ \frac{1}{Z_1} \right]$$

KCL at node 6:

$$\frac{V_6 - V_3}{Z_2} + \frac{V_6}{Z_3} + \frac{V_6 - V_5}{R_0} = 0$$

[5.0]

$$V_3 \left[ \frac{-1}{Z_2} \right] + V_5 \left[ \frac{-1}{R_0} \right] + V_6 \left[ \frac{1}{Z_2} + \frac{1}{Z_3} + \frac{1}{R_0} \right] = 0$$

But  $V_5$  is a function of  $V_3$  and the open-loop gain,

$$V_5 = V_3 \left[ \frac{j|GB|}{f} \right]$$

so now we have

[5.1]

$$V_3 \left[ \frac{-1}{Z_2} - \frac{j|GB|}{R_0 f} \right] + V_6 \left[ \frac{1}{Z_2} + \frac{1}{Z_3} + \frac{1}{R_0} \right] = 0$$

Collect equations 4.1 and 5.1 into a matrix for solving.

$$\begin{bmatrix} \frac{1}{Z_1} + \frac{1}{Z_2} + j\omega C_0 & \frac{-1}{Z_2} \\ \frac{-1}{Z_2} - \frac{j|GB|}{R_0 f} & \frac{1}{Z_2} + \frac{1}{Z_3} + \frac{1}{R_0} \end{bmatrix} \begin{bmatrix} V_3 \\ V_6 \end{bmatrix} = \begin{bmatrix} \frac{1}{Z_1} V_1 \\ 0 \end{bmatrix}$$

(4.1)

(5.1)

(3)

For a general  $2 \times 2$  system, the matrix can be reduced to triangular form by the series of row operations

$$\begin{bmatrix} A & B & | & E \\ C & D & | & F \end{bmatrix} \sim \begin{bmatrix} 1 & B/A & | & E/A \\ -1 & -D/A & | & -F/A \end{bmatrix} \sim \begin{bmatrix} 1 & B/A & | & E/A \\ 0 & B/A - D/A & | & E/A - F/A \end{bmatrix} \sim \begin{bmatrix} 1 & B/A & | & E/A \\ 0 & 1 & | & \left( \frac{E/A - F/A}{B/A - D/A} \right) \end{bmatrix}$$

So for the AC circuit system, the output voltage is given by

[6a] 
$$V_o = \frac{\frac{E}{A} - \frac{F}{C}}{\frac{B}{A} - \frac{D}{C}} = \frac{E - \frac{FA}{C}}{B - \frac{DA}{C}}$$

where

$$A = \frac{1}{Z_1} + \frac{1}{Z_2} + j\omega C_0$$

$$B = \frac{-1}{Z_2}$$

[6.b] 
$$C = \frac{-1}{Z_2} = j \frac{|GB|}{R_0 f} = \frac{-R_0 f - j Z_2 |GB|}{Z_2 R_0 f}$$

$$D = \frac{1}{Z_2} + \frac{1}{Z_3} + \frac{1}{R_0} \approx \frac{1}{Z_2} + \frac{1}{Z_3}$$

$$E = \frac{1}{Z_1} V_i$$

$$F = 0$$

Substituting in E and F gives us a gain equation

$$V_o = \frac{\frac{1}{Z_1} V_i - 0}{B - \frac{DA}{C}}$$

[7.0] 
$$A_v = \frac{1}{Z_1 (B - \frac{DA}{C})}$$

Getting the expression  $B - \frac{DA}{C}$  in an appropriate form takes some algebra.

$$\begin{aligned} -\frac{DA}{C} &= DA(-C^{-1}) = \left[ \frac{1}{Z_2} + \frac{1}{Z_3} \right] \left[ \frac{1}{Z_1} + \frac{1}{Z_2} + j\omega C_0 \right] \left[ \frac{Z_2 R_0 f}{R_0 f + j Z_2 |GB|} \right] \\ &= \left[ \frac{R_0 f}{j Z_2 |GB|} \left( \frac{Z_2}{1 - j \frac{R_0 f}{Z_2 |GB|}} \right) \right] \left[ \frac{Z_2 + Z_3}{Z_2 Z_3} \right] \left[ \frac{1}{Z_1 || Z_2 + j\omega C_0} \right] \end{aligned}$$

$$\frac{-DA}{C} = \frac{-j R_o f}{Z_2 |GB|} \left( \frac{1}{1 - j \frac{R_o f}{Z_2 |GB|}} \right) \left[ \frac{Z_2 + Z_3}{-Z_3} \right] \left[ \frac{Z_1 + Z_2}{Z_1 Z_2} \right] (1 + j \omega C_o (Z_1 \parallel Z_2))$$

Next  $B - \frac{DA}{C}$

$$\begin{aligned} B - \frac{DA}{C} &= \frac{-1}{Z_2} - j \frac{R_o f}{Z_2 |GB|} \left( \frac{Z_2 + Z_3}{Z_3} \right) \left( \frac{Z_1 + Z_2}{Z_1 Z_2} \right) (1 + j \omega C_o Z_1 \parallel Z_2) \left( \frac{1}{1 - j \frac{R_o f}{Z_2 |GB|}} \right) \\ &= \frac{-1}{Z_2} \left[ 1 + j \frac{R_o f}{Z_2 |GB|} \left( \frac{Z_2 + Z_3}{Z_3} \right) \left( \frac{Z_1 + Z_2}{Z_1} \right) (1 + j \omega C_o Z_1 \parallel Z_2) \left( \frac{1}{1 - j \frac{R_o f}{Z_2 |GB|}} \right) \right] \end{aligned}$$

and the whole transfer function is

$$[7.1] \quad A_v = \frac{-Z_2}{Z_1} \left[ \frac{1}{1 + j \frac{f R_o (Z_1 + Z_2)(Z_2 + Z_3)}{|GB| Z_1 Z_2 Z_3} \left[ \frac{1 + j \omega C_o Z_1 \parallel Z_2}{1 - j \frac{R_o f}{Z_2 |GB|}} \right]} \right]$$

where

$$(1a, 2a, 3a) \quad Z_1 = R_1 \left[ 1 - j \frac{\omega}{\omega_1} \right], \quad Z_2 = R_2 \left[ \frac{1}{1 + j \frac{\omega}{\omega_2}} \right], \quad Z_3 = R_3 \left[ 1 - j \frac{\omega}{\omega_3} \right]$$

and

$$(1b, 2b, 3b) \quad \omega_1 = \frac{1}{R_1 C_1}, \quad \omega_2 = \frac{1}{R_2 C_2}, \quad \omega_3 = \frac{1}{R_3 C_3}$$

op-amp.c

The frequency response of the circuit with a set of values for  $\{C_o, R_1, R_2, R_3, C_1, C_2, C_3\}$  and the LM7171 opamp can be quickly evaluated using the C script op-amp.c. You also need the lm7171.cir NgSpice model, gnuplot C interface header/linker/compilation files, and optionally experimental data with row format:

Freq dB Phase(radians)

Dependencies are NgSpice, GNU Scientific Library, and GNU Plot.


\$ make

\$ ./op-amp 20 1 10 1 330 2 330

ngspice 2 -> quit <enter>



5
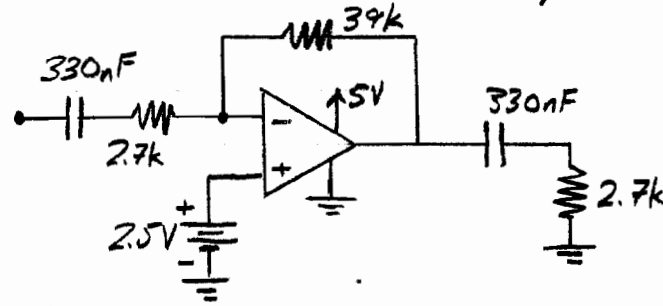
# Experimental, Theoretical, and Spice Results





Gussed Values for  
op\_amp.c:  
 $|G| = 35 \text{ MHz}$   
 $R_0 = 20 \Omega$   
 $C_0 = 500 \text{ pF}$

Circuit Constructed on Breadboard

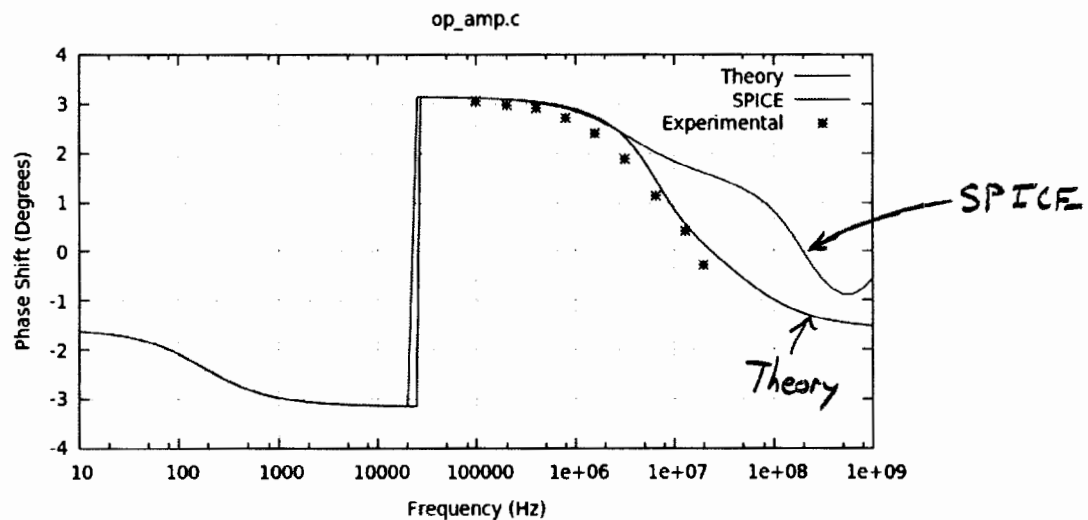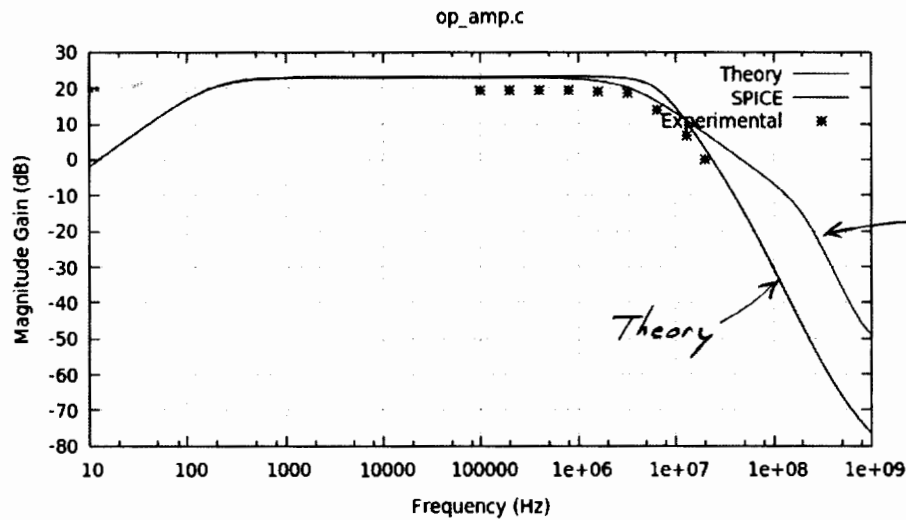

6

# Oscillations and Stability

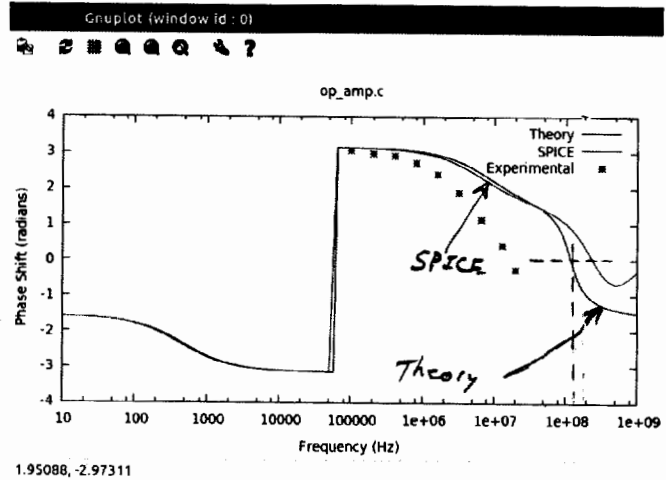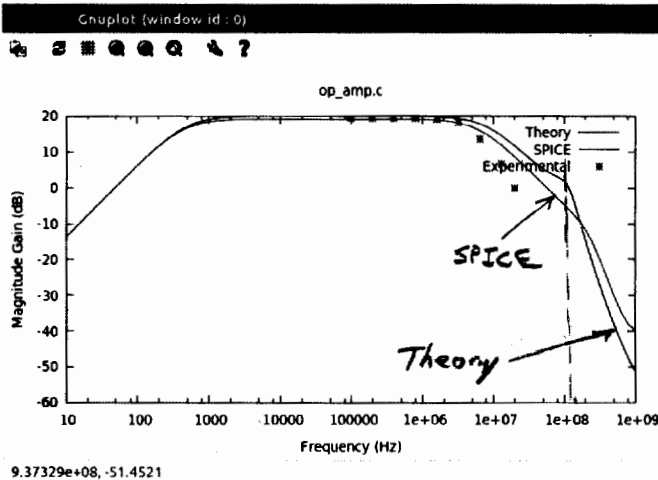

Look at the simulation with the values in the table. The phase shift crosses zero at about 100 MHz. On the magnitude plot, there is a resonance peak/shoulder at this positive-feedback frequency (100 MHz) whose peak is above zero. I.e. greater than unity positive feedback = oscillation at 100 MHz.

$C_0$	100 pF
$R_1$	1 k $\Omega$
$R_2$	10 k $\Omega$
$R_3$	1 k $\Omega$
$C_1$	330 nF
$C_2$	2 pF
$C_3$	330 nF

For analyze/design for stability, it would be helpful to develop a script for generating Nyquist plots for different component values.

For Nyquist plots, we usually want the closed loop transfer function in the form

[8.0]

$$A_v(s) = \frac{A(s)}{1 + L(s)}$$

where  $A(s)$  is a complex polynomial and  $L(s)$  is a rational function  $L(s) = \frac{P(s)}{Q(s)}$ , or a fraction of the polynomials.

(7)

So that we can analyze when the characteristic equation has a root (is zero) in the right half plane (or along the sinusoidal  $j\omega$ -axis).

$$F(s) = 1 + L(s) = 0$$

But we're getting ahead of ourselves; first we need  $A_v$  in the form of eq. 8.0. Starting with equation 7.1, we can assume that the poles  $\omega_1$  and  $\omega_3$  are negligible for high frequency and stability analysis.

[8.1]

$$A_v = \frac{-Z_2}{R_1} \left[ \frac{1}{1 + \frac{j\omega R_0 (R_1 + Z_2)(Z_2 + R_3)}{|GB| R_1 Z_2 R_3} \left[ \frac{1 + j\omega C_0 (R_1 \| Z_2)}{1 - j \frac{R_0 \omega}{Z_2 |GB|}} \right]} \right]$$

We can expand  $R_1 \| Z_2$  and  $\frac{Z_2 + R_3}{R_3}$  and  $Z_2$  using equation 2a

$$R_1 \| Z_2 = \frac{R_1 Z_2}{R_1 + Z_2} = \frac{R_1 R_2}{(1 + j\frac{\omega}{\omega_2})(R_1 + \frac{R_2}{1 + j\frac{\omega}{\omega_2}})} = \frac{R_1 R_2}{R_1(1 + j\frac{\omega}{\omega_2}) + R_2}$$

$$\frac{Z_2 + R_3}{R_3} = \frac{R_2}{R_3(1 + j\frac{\omega}{\omega_2})} + 1 = \frac{R_2 + R_3(1 + j\frac{\omega}{\omega_2})}{R_3(1 + j\frac{\omega}{\omega_2})}$$

[8.2]

$$A_v = \frac{-Z_2}{R_1} \left[ \frac{1}{1 + \frac{j\omega R_0 [R_1(1 + j\frac{\omega}{\omega_2}) + R_2] [R_2 + R_3(1 + j\frac{\omega}{\omega_2})]}{(2\pi |GB| \cdot R_2) R_1 \cdot R_3(1 + j\frac{\omega}{\omega_2})} \left[ \frac{1 + j\omega C_0 \left[ \frac{R_1 R_2}{R_1(1 + j\frac{\omega}{\omega_2})} + R_2 \right]}{1 - j \frac{R_0 \omega (1 + j\frac{\omega}{\omega_2})}{R_2 \cdot 2\pi |GB|}} \right]} \right]$$

Next we define  $\omega_0$  and  $\omega_4$  as

[9]

$$\omega_0 = \frac{2\pi |GB| R_2}{R_0}$$

[10]

$$\omega_4 = \frac{1}{R_2 C_0}$$

so that

[8.3]

$$A_v = \frac{-R_2}{R_1(1 + j\frac{\omega}{\omega_2})} \left[ \frac{1}{1 + \frac{j\omega [R_1(1 + j\frac{\omega}{\omega_2}) + R_2] [R_2 + R_3(1 + j\frac{\omega}{\omega_2})]}{\omega_0 \cdot R_1 \cdot R_3(1 + j\frac{\omega}{\omega_2})} \left[ \frac{1 + j\frac{\omega}{\omega_4} \left( \frac{R_1}{R_1(1 + j\frac{\omega}{\omega_2})} + R_2 \right)}{1 - j\frac{\omega}{\omega_0} (1 + j\frac{\omega}{\omega_2})} \right]} \right]$$

Next we distribute the term  $(1+j\omega\omega_2)$  into the large square bracket and the term  $\frac{[R_1(1+j\omega\omega_1)+R_2]}{R_1}$  into the second bracket.

$$[8.4] \quad A_0 = \frac{-R_2}{R_1} \left[ \frac{1}{1+j\frac{\omega}{\omega_2} + j\frac{\omega}{\omega_0 R_3} [R_2+R_3(1+j\frac{\omega}{\omega_2})]} \left[ \frac{\frac{R_1(1+j\frac{\omega}{\omega_1})+R_2}{R_1} + j\frac{\omega}{\omega_4}}{1-j\frac{\omega}{\omega_0}(1+j\frac{\omega}{\omega_2})} \right] \right]$$

Now we are ready to define  $L$  as

$$[8.5] \quad L = j\frac{\omega}{\omega_2} + j\frac{\omega}{\omega_0 R_3} [R_2+R_3(1+j\frac{\omega}{\omega_2})] \left[ \frac{\frac{R_2}{R_1}+1+j\frac{\omega}{\omega_2} + j\frac{\omega}{\omega_4}}{1-j\frac{\omega}{\omega_0} + \frac{\omega^2}{\omega_0\omega_2}} \right]$$

$$[8.6] \quad L = j\frac{\omega}{\omega_2} + j\frac{\omega}{\omega_0} \left[ \left( \frac{R_2}{R_3}+1 \right) + j\frac{\omega}{\omega_2} \right] \left[ \left( \frac{R_2}{R_1}+1 \right) + j\omega \left( \frac{1}{\omega_2} + \frac{1}{\omega_4} \right) \right] \left[ \left( 1 + \frac{\omega^2}{\omega_0\omega_2} \right) - j\frac{\omega}{\omega_0} \right]$$

$$[8.7] \quad L = j\omega \left[ \frac{1}{\omega_2} + \frac{\left[ \left( \frac{R_2}{R_3}+1 \right) + j\frac{\omega}{\omega_2} \right] \left[ \left( \frac{R_2}{R_1}+1 \right) + j\omega \left( \frac{1}{\omega_2} + \frac{1}{\omega_4} \right) \right]}{\left[ \omega_0 + \frac{\omega^2}{\omega_2} - j\omega \right]} \right]$$

$$[8.8] \quad L = j\frac{\omega}{\omega_2} \left[ 1 + \frac{\left[ \left( \frac{R_2}{R_3}+1 \right) + j\frac{\omega}{\omega_2} \right] \left[ \left( \frac{R_2}{R_1}+1 \right) + j\omega \left( \frac{\omega_2+\omega_4}{\omega_2\omega_4} \right) \right]}{\frac{\omega_0}{\omega_2} + \frac{\omega^2}{\omega_2^2} - j\frac{\omega}{\omega_2}} \right]$$

$$[8.9] \quad L = j\frac{\omega}{\omega_2} \left[ \frac{\left[ \frac{\omega^2}{\omega_2^2} - j\frac{\omega}{\omega_2} + \frac{\omega_0}{\omega_2} \right] + \left[ \frac{R_2+R_3}{R_3} + j\frac{\omega}{\omega_2} \right] \left[ \frac{R_2+R_1}{R_1} + j\omega \left( \frac{\omega_2+\omega_4}{\omega_2\omega_4} \right) \right]}{\frac{\omega^2}{\omega_2^2} - j\frac{\omega}{\omega_2} + \frac{\omega_0}{\omega_2}} \right]$$

~~Considering just the numerator  $P(s)$  after distributing the outer  $j\omega$ ,~~

$$P(j\omega) = \frac{j\omega^3}{\omega_0\omega_2^2} + \frac{\omega^2}{\omega_2^2} + j\frac{\omega\omega_0}{\omega_2} + \left[ \frac{j\omega(R_2+R_3)}{\omega_2 R_3} - \frac{\omega}{\omega_2} \right]$$



[P.10]

$$L = \frac{\frac{j\omega^3}{\omega_2^2} + \frac{\omega^2}{\omega_2} + \frac{j\omega\omega_0}{\omega_2} + \left[ \frac{j\omega(R_2+R_3)}{R_3} - \frac{\omega^2}{\omega_2} \right] \left[ \frac{R_2+R_1}{R_1} + j\omega \left( \frac{\omega_2+\omega_4}{\omega_2\omega_4} \right) \right]}{\frac{\omega^2}{\omega_2} - j\omega + \omega_0}$$

Breaking  $L$  into two components and converting to  $s$ -domain,  
 $s = j\omega$ ,  $s^2 = -\omega^2$ ,  $s^3 = -j\omega^3$ .

$$Q(s) = \frac{-1}{\omega_2} s^2 - s + \omega_0$$

$$P(s) = \frac{-s^3}{\omega_2^2} - \frac{s^2}{\omega_2} + \frac{s\omega_0}{\omega_2} + \left[ \frac{s(R_2+R_3)}{R_3} + \frac{s^2}{\omega_2} \right] \left[ \frac{R_1+R_2}{R_1} + s \left( \frac{\omega_2+\omega_4}{\omega_2\omega_4} \right) \right]$$

$$P(s) = \frac{-s^3}{\omega_2^2} - \frac{s^2}{\omega_2} + \frac{s\omega_0}{\omega_2} + \frac{s(R_2+R_3)(R_1+R_2)}{R_1 R_3} + \frac{s^2(R_2+R_3)(\omega_2+\omega_4)}{R_3 \omega_2 \omega_4} \\ + \frac{s^2(R_1+R_2)}{\omega_2 R_1} + \frac{s^3(\omega_2+\omega_4)}{\omega_2^2 \omega_4}$$

$$P(s) = s^3 \left[ \frac{\omega_2+\omega_4}{\omega_2^2 \omega_4} - \frac{1}{\omega_2^2} \right] + s^2 \left[ \frac{(R_2+R_3)(\omega_2+\omega_4)}{R_3 \omega_2 \omega_4} + \frac{(R_1+R_2)}{\omega_2 R_1} - \frac{1}{\omega_2} \right] \\ + s \left[ \frac{\omega_0}{\omega_2} + \frac{(R_2+R_3)(R_1+R_2)}{R_1 R_3} \right]$$

$$P(s) = s^3 \left[ \frac{1}{\omega_2^2} \left( \frac{\omega_2+\omega_4}{\omega_4} - \frac{\omega_4}{\omega_4} \right) \right] + s^2 \left[ \frac{1}{\omega_2} \left( \frac{R_1+R_2}{R_1} - \frac{R_1}{R_1} + \frac{(R_2+R_3)(\omega_2+\omega_4)}{R_3 \omega_4} \right) \right] \\ + s \left[ \frac{\omega_0}{\omega_2} + \frac{(R_2+R_3)(R_1+R_2)}{R_1 R_3} \right]$$

So finally we have

[11]

$$L(s) = \frac{As^3 + Bs^2 + Ds}{Es^2 + Gs + \omega_0} \quad \text{where}$$

[11a]

$$A = \frac{1}{\omega_2 \omega_4}$$

[11b]

$$B = \frac{1}{\omega_2} \left[ \frac{R_2}{R_1} + \frac{(R_2+R_3)(\omega_2+\omega_4)}{R_3 \omega_4} \right],$$

[11d]

$$D = \frac{\omega_0}{\omega_2} + \frac{(R_1+R_2)(R_2+R_3)}{R_1 R_3},$$

[11e, 11g]

$$E = \frac{-1}{\omega_2},$$

$$G = -1$$

$$\text{such that } A_0 = \frac{-R_2}{R_1} \left[ \frac{1}{1 + L(s)} \right]$$

Re-expanding the gain equation for scripting

[8.11]

$$A_v = \frac{-R_2}{R_1} \left[ \frac{1}{1+L(s)} \right] = \frac{-R_2}{R_1} \left[ \frac{1}{1 + \frac{-j\omega^3/\omega_2 - \omega^2 B + j\omega D}{\frac{\omega^2}{\omega_2} + j\omega + \omega_0}} \right]$$

[11.2]

$$L(\omega) = \frac{-j\frac{\omega^3}{\omega_2} - B\omega^2 + j\omega D}{\frac{\omega^2}{\omega_2} + j\omega + \omega_0} = \frac{-B\omega^2 - j(\frac{\omega^3}{\omega_2} - \omega D)}{(\frac{\omega^2}{\omega_2} + \omega_0) + j\omega}$$

Equations 8.11 and 11.2 should work for evaluating Bode and Nyquist plots on the computer, but we might be able to glean more insight by hand.

The system becomes unstable when the characteristic equation is 0,

[12]

$$F(s) = 1 + L(s) = 0$$

ie. if there are any roots of  $F(s)$  on the right-half  $s$ -plane.

We can expand  $F(s)$

$$F(s) = 1 + L(s) = 1 + \frac{P(s)}{Q(s)} = \frac{Q(s) + P(s)}{Q(s)}$$

$$F(s) = \frac{As^3 + (B+E)s^2 + (D+G)s + \omega_0}{Es^2 + Gs + \omega_0}$$

$$F(s) = \frac{\left[\frac{1}{\omega_2}\right]s^3 + \left[\frac{R_2}{R_1\omega_2} + \frac{(R_2+R_3)(\omega_2+\omega_4)}{R_3\omega_4\omega_2} - \frac{1}{\omega_2}\right]s^2 + \left[\frac{\omega_0}{\omega_2} + \frac{(R_1+R_2)(R_2+R_3)}{R_1R_3} - 1\right]s + \omega_0}{\frac{-1}{\omega_2}s^2 - s + \omega_0}$$

Multiply through by  $\frac{\omega_2}{\omega_2}$  and going back to  $j\omega$ -domain

$$F(j\omega) = \frac{-j\omega^3 - \omega^2 \left[ \frac{R_2}{R_1} - 1 + \frac{(R_2+R_3)(\omega_2+\omega_4)}{R_3\omega_4} \right] + j\omega \left[ \omega_0 - \omega_2 \left( 1 - \frac{(R_1+R_2)(R_2+R_3)}{R_1R_3} \right) \right] + \omega_0}{\omega^2 - j\omega + \omega_0}$$