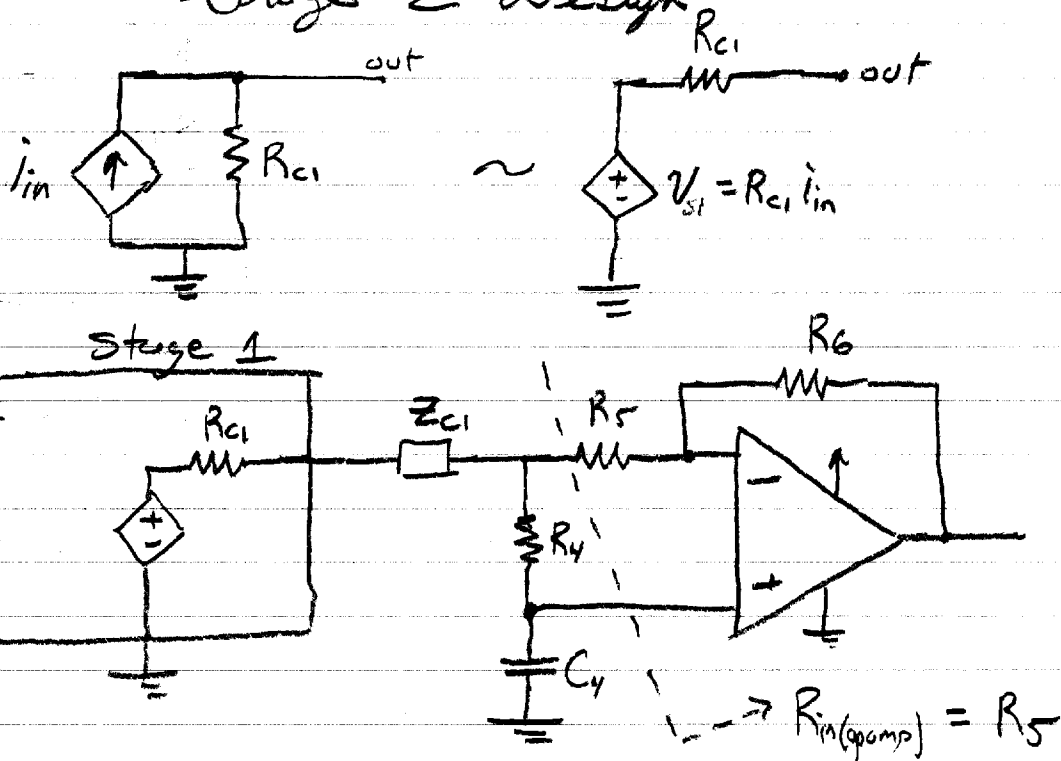


## Stage 2 Design



For now, let  $Z_{c1}$  be a short. In the future we may want a finite load for noise.

$$Z_{c1} = \emptyset$$

The parallel combination of the  $R_4, C_4$  low pass filter and the op amp input resistance  $R_5$  should not significantly load stage 1.

$$R_5 \parallel R_4 \geq 10 R_{c1}$$

The  $R_4, C_4$  low pass filter should filter out the operating frequency to provide a stable reference voltage to the op-amp.

$$\omega_4 \leq \frac{1}{10} \omega_{op}$$

$$\omega_4 = \frac{1}{R_4 C_4} \leq \frac{1}{10} \cdot 2\pi f_{op}$$

If we design  $R_4 = 10 R_5$ , then

$$R_5 = 10 R_{c1}, \quad R_4 = 100 R_{c1}, \quad C_4 \geq \frac{5}{\pi R_4 f_4}$$

where  $f_4$  should be set well below the signal freq