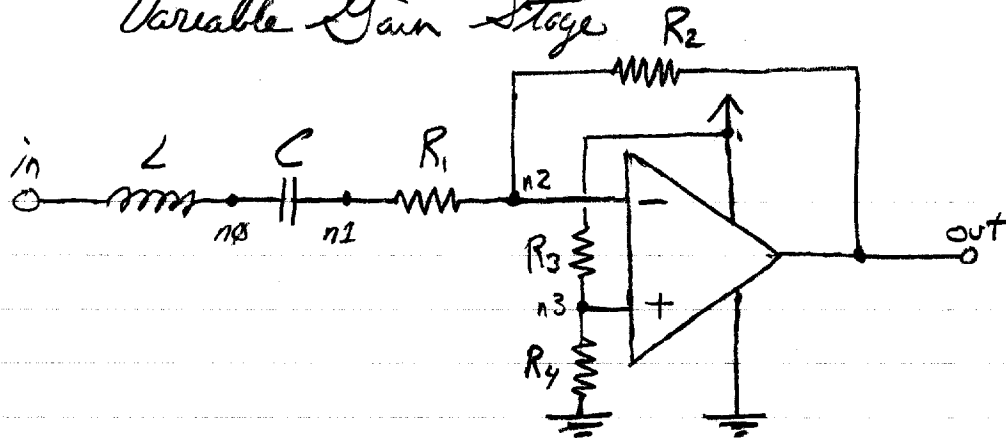


①

## Variable Gain Stage



KCL at node n2: 
$$\frac{V_{IN} - V_2}{Z_{LCR}} = \frac{V_2 - V_{OUT}}{R_2}$$

For an ideal op-amp,  $V_2 = V_3 = \text{Constant}$ , so from AC point of view  $V_2 = 0$

and we are left with 
$$\frac{V_{IN}}{Z_{LCR}} = \frac{-V_{OUT}}{R_2}$$

or 
$$\frac{V_{OUT}}{V_{IN}} = \frac{-R_2}{Z_{LCR}}$$

The series impedance of L, C, and R<sub>1</sub> is

$$\begin{aligned} Z_{LCR} &= j\omega L + \frac{1}{j\omega C} + R_1 = R_1 + j\left(\omega L - \frac{1}{\omega C}\right) = R_1 \left(1 + j\left(\frac{\omega L}{R_1} - \frac{1}{\omega R_1 C}\right)\right) \\ &= R_1 \left(1 + j\left(\frac{\omega}{\omega_{HP}} - \frac{\omega_{LP}}{\omega}\right)\right) = R_1 \sqrt{1 + \left(\frac{\omega}{\omega_{HP}}\right)^2 + \left(\frac{\omega_{LP}}{\omega}\right)^2} e^{j \tan^{-1}\left(\frac{\omega}{\omega_{HP}} - \frac{\omega_{LP}}{\omega}\right)} \end{aligned}$$

So for this op-amp stage, the gain and input impedance are

$$\frac{V_{OUT}}{V_{IN}} = \frac{-R_2}{R_1} \left( \frac{1}{\sqrt{1 + \left(\frac{\omega_{LP}}{\omega}\right)^2 + \left(\frac{\omega}{\omega_{HP}}\right)^2}} \right) \cdot e^{-j \tan^{-1}\left(\frac{\omega}{\omega_{HP}} - \frac{\omega_{LP}}{\omega}\right)}$$

and

$$|Z_{in}| = R_1 \sqrt{1 + \left(\frac{\omega_{LP}}{\omega}\right)^2 + \left(\frac{\omega}{\omega_{HP}}\right)^2}$$

where

$$\omega_{LP} = \frac{1}{R_1 C} \quad \text{and} \quad \omega_{HP} = \frac{R_1}{L}$$

(2)

The input impedance should be set so as not to heavily load the prior stage.

$$R_i \geq 10 \cdot R_{out}$$

Then the two reactive coupling components are set

$$C = \frac{1}{2\pi R_i f_{LP}}$$

$$L = \frac{R_i}{2\pi f_{HP}}$$

In practice we usually want  $f_{LP} \leq \frac{1}{10} f_{min}$  and  $f_{HP} \geq 10 f_{max}$ , so

$$f_{LP} \leq \frac{1}{10} f_{min}$$

$$f_{HP} \geq 10 f_{max}$$

$$\omega_{LP} \leq \frac{2\pi}{10} f_{min}$$

$$\omega_{HP} \geq 20\pi f_{max}$$

$$\frac{1}{R_i C} \leq \frac{2\pi}{10} f_{min}$$

$$\frac{R_i}{L} \geq 20\pi f_{max}$$

$$R_i C \geq \frac{10}{2\pi f_{min}}$$

$$\frac{L}{R_i} \leq \frac{1}{20\pi f_{max}}$$

$$C \geq \frac{10}{2\pi f_{min} R_i} \quad \text{and} \quad L \leq \frac{R_i}{20\pi f_{max}}$$

Within the bandpass region, the desired gain is achieved with

$$R_2 = \frac{\text{Gain}}{R_i}$$

Also FFL, the output resistance of the op-amp stage is that of the op-amp itself, in parallel with  $R_2$

$$R_{out} = R_{o(\text{op-amp})} \parallel R_2 \approx R_{o(\text{op-amp})}$$