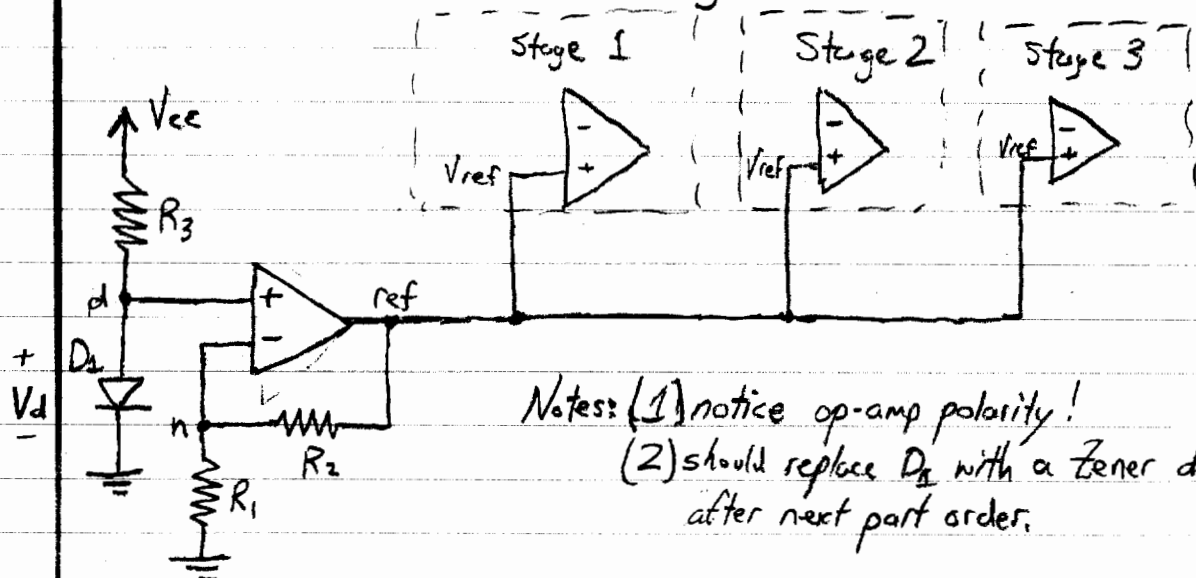


Reducing Noise and Feedback of Op Amp Stages with a constant voltage reference



Notes: (1) notice op-amp polarity!

(2) should replace D_1 with a Zener diode after next part order.

For ideal opamp, $V_d = V_n$.

Taking $2\pi f$ at node n:

$$\frac{V_n}{R_1} = \frac{V_{ref} - V_n}{R_2}$$

rearranging and replacing $V_n = V_d$

$$V_d \left[\frac{1}{R_1} + \frac{1}{R_2} \right] = V_{ref} \left[\frac{1}{R_2} \right]$$

$$V_{ref} = \left[1 + \frac{R_2}{R_1} \right] V_d$$

Designing R_1, R_2 : $R_1 = \frac{R_1 + R_2}{V_{ref}} V_d$

Let $R_1 + R_2 = 5k$ for 1mA bias.

$$R_1 = 5k\Omega \left(\frac{V_d}{V_{ref}} \right)$$

$$R_2 = 5k\Omega \left(1 - \frac{V_d}{V_{ref}} \right)$$

$$\approx 5k \cdot \frac{0.7}{2.5} = 1.4k\Omega$$

$$\approx 5k \left(1 - \frac{0.7}{2.5} \right) = 3.6k\Omega$$

Choose R_3 to not waste too much current.

$$R_3 = 10k\Omega$$